
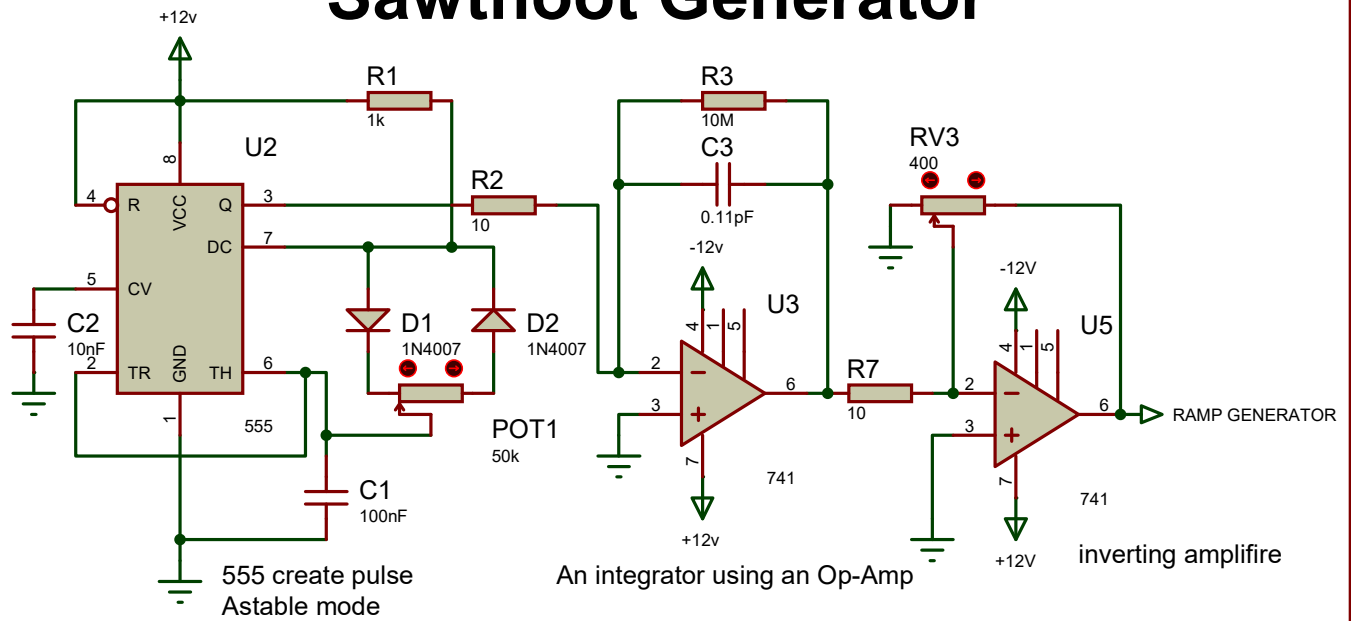



Sawthoot Generator

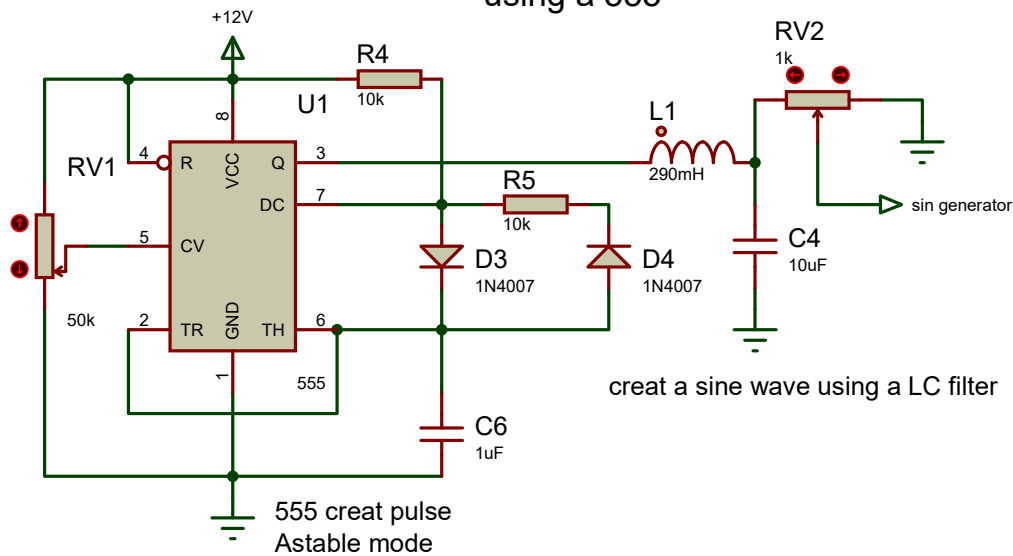

sin generator $f = 1/(2\pi \cdot L \cdot C)$ using a 555



comparator

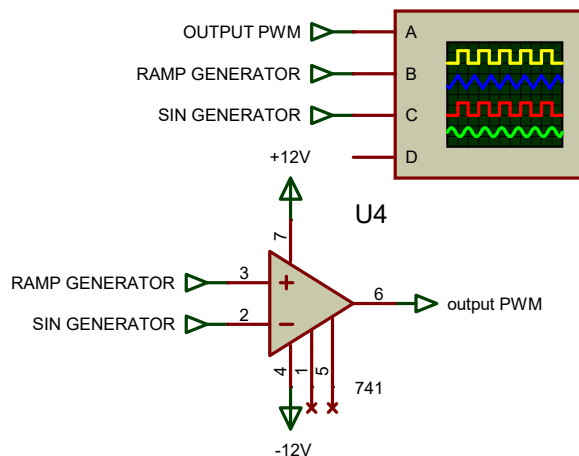

PWM modulation Pulse & Technik Project

simulated by:
Alireza Sotoodeh
Date: spring 1404