

# stage3) Encoding

desinged by: Alireza Sotoodeh

in this stage by using transistor (Cmos/jFet) or switching IC  
(like 4066 or 4016) and optocouplers, we can creat Encoder!

the only reason i used optocouplers was due to thier high switching capability

